

期末复习

2024. 1. 8

考试题型

- 名词解释: $6 \times 2 \text{分} = 12 \text{分}$ (IC CMOS PMOS NMOS ...)
- 选择: $11 \times 2 \text{分} = 22 \text{分}$
- 解答题: $5 \times X \text{分} = 66 \text{分}$ (Analog 2, Digital 2, Layout 1)
 - 模拟小信号模型与计算
 - 看版图, 从版图画出 Schematic
 - 从布尔函数到数字逻辑门
 - 多输入逻辑门延时计算

主要内容 (1)

Creativity + Design + Verification

每两年单位面积上的晶体管数量增一倍

- Technology scaling down (digital driven) with Moore's Law

But in recent decade more SoC, SiP and Chiplets

- Analog & Digital Design Flow (Transistor level vs. Behavior-RTL)

行为级 - RTL (传输级)

- Analog vs. Digital with technology scaling down


功耗在降低

- I/V curve and operation region of MOSFET

$$I_D = \mu_n C_{OX} \frac{W}{L} \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right] \quad I_D = \frac{1}{2} \mu_n C_{OX} \frac{W}{L} (V_{GS} - V_{TH})^2$$

- Diode and its capacitance
 
$$C_j = \frac{C_{j0}}{(1 - V_D / \phi_0)^m}$$



主要内容 (2) 跨导系数 $\beta = \mu_n C_{ox} \frac{W}{L}$

- Body Effect & Channel Length Modulation & **Weak inversion**

$$V_{TH} = V_{TH0} + \gamma \left(\sqrt{|2\Phi_F + V_{SB}|} - \sqrt{|2\Phi_F|} \right)$$

$$I_D \approx \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$I_D = I_0 \exp \frac{V_{GS}}{\zeta V_T}$$

$$I_D = I_s \left(e^{\frac{V_D}{\phi_T}} - 1 \right) \quad \phi_T = \frac{kT}{q} = 26 \text{ mV } (300\text{K})$$

- Small Signal Model

管子是一个压控电流源，主要由 V_{GS} 控制，受到 V_{DS} 的影响



Single-Page MOSFET Model

$$I_{DS} = K'_n \frac{W}{L} (V_{GS} - V_T)^2$$

$$V_{GS} - V_T \approx 0.2 \text{ V}$$

$$\begin{aligned} K'_n &\approx 100 \mu\text{A/V}^2 \\ K'_p &\approx 40 \mu\text{A/V}^2 \end{aligned}$$

$$K'_n = \frac{1}{2} \mu_n C_{ox}$$

$$g_m = 2K'_n \frac{W}{L} (V_{GS} - V_T) = 2 \sqrt{K'_n \frac{W}{L} I_{DS}} = \frac{2 I_{DS}}{V_{GS} - V_T}$$

$$r_{DS} = r_o = \frac{V_{EL} \rightarrow E_n}{I_{DS}}$$

$$V_{En} \approx 5 \text{ V}/\mu\text{mL} \quad V_{Ep} \approx 8 \text{ V}/\mu\text{mL}$$

$$v_{sat} = 10^7 \text{ cm/s}$$

$$f_T = \frac{1}{2\pi} \frac{3}{2n} \frac{\mu}{L^2} (V_{GS} - V_T) \quad \text{or now } \approx \frac{v_{sat}}{2\pi L}$$

$$y = \frac{g_{mb}}{g_m} = \frac{\gamma}{2\sqrt{2\phi_F + V_{BS}}}$$

$$g_{mb} = g_m \frac{\gamma}{2\sqrt{2\phi_F + V_{BS}}}$$

$$= g_m \cdot y$$

$$g_{mb} = g_m \cdot \frac{\gamma}{2\sqrt{2\phi_F + V_{BS}}} \quad R_{on} \text{ (大信号)}$$

$$r_o = \frac{1}{I_D \lambda}$$

小信号

$$f_T = \frac{g_m}{2\pi C_{GS}}$$

$$\lambda = \frac{1}{V_E \cdot L}$$

$$\sqrt{2\mu_0 C_{ox} \left(\frac{W}{L}\right) I_D}$$

Willy Sansen 10-05 0170

$$g_{ds} = \frac{1}{r_o} = \lambda I_D$$

FF 高频 SS 低频,

主要内容 (3)

- PVT variation of parameters: (+) R , g_m , speed... (-) V_{th} , V_{be} ...

- Process Steps: → 图片、

1. Wafer preparation: produce the proper type of substrate

2. Lithography (defines the geometry) photolithography 光刻

3. Oxidation, 氧化

4. 扩散 Diffusion, 离子注入 Ion implantations, 沉积 Deposition

5. Etching (2-5) 不断循环



6. Planarization 平坦化

- DRC (minimum distance, matching etc.) LVS (Layout vs Schematic)

主要内容 (4)

- Layout: from Layout to schematic
- Matching: **identical cells** are good for matching

(用多个一样的-电流镜)

  

- Two dimensional matching (交差摆放-差分对)

对称分布

主要内容 (5)

开关 \Rightarrow 线性区

$$r_{ON} = \frac{1}{\left. \frac{\partial i_D}{\partial v_{DS}} \right|_Q}$$

- Switch (charge feedthrough) in linear:

$$= \frac{L}{K'W(V_{GS} - V_{TH} - V_{DS})}$$

- Active resistor (diode connected transistor) in saturation ($1/gm$)



- Current mirror: 一个由二极管连接的管子控制栅极的管子: r_{ds}

- Cascode current mirror: 输出阻抗被提升至 r_{ds} 的 $(gm \cdot r_{ds})$ 倍
 $gm \cdot r_{ds}$ 为上面管子的本征增益, PMOS则相反, 为下面管子

- 一些电压关系计算, 压低最小输出电压

主要内容 (6)

$$A_v = -g_m \cdot R_D$$

v_{in} of I_D



- **Common-Source Stage**

- Inverse Gain \rightarrow I-V curve (why $R_D < r_o$ of transistor)
- 增益等于输入管 g_m * 输出节点的阻抗 (上下并联) ✱

- **Source Follower**

$$G_m = g_m / (1 + g_m \cdot R_S)$$

With ^{low} ~~high~~ output resistance
Similar to Cascode

- **Common-Gate Stage**

Current input with $(1/g_m)$ \rightarrow $i_{out} = i_{in}$

With low input resistance: $1/g_m$

主要内容 (7) $I_C = I_S \exp(V_{BE}/V_t)$

$\downarrow 2\text{mV}/^\circ\text{C}$
 $\nearrow 0.085\text{mV}/^\circ\text{C}^2$

- Bandgap reference (ZTC = PTAT+CTAT)

$$V_{REF} = V_{BE} + KV_t$$


proportional to
the absolute temperature.

$$V_{ref} = V_{EB3} + I \times LR$$

$$= V_{EB3} + \frac{V_t \ln K}{R} \times LR$$

$$= V_{EB3} + LV_t \ln K$$

随温度化后不变

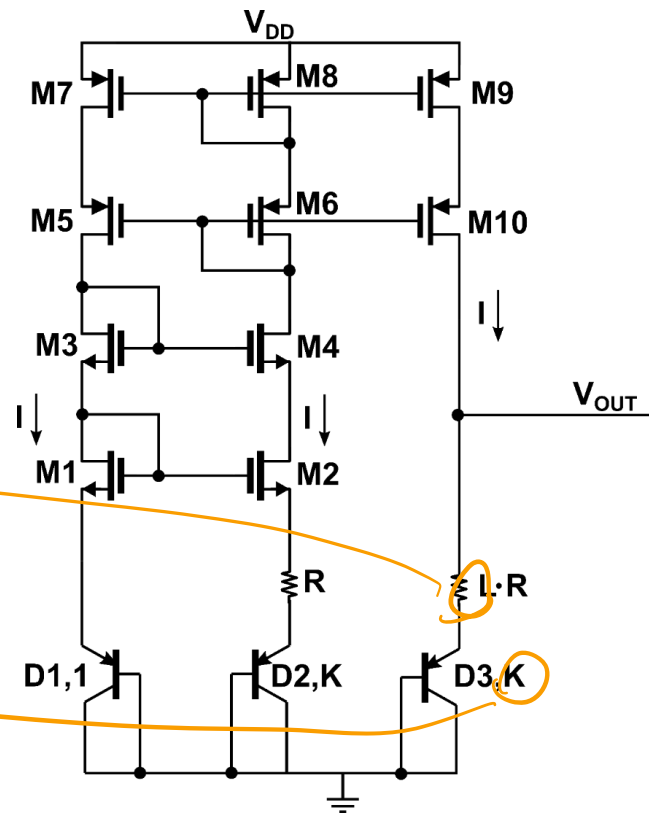

主要内容 (8)

对电源噪声的稳定性问题

$$CMRR = \left| \frac{A_{DM}}{A_{CM-DM}} \right|$$

- A differential signal is better in PSRR/Interference
- Virtual ground at node P with fixed I_{SS}

• $V_{in,CM}$ Range:


$$V_{GS1} + (V_{GS3} - V_{TH3}) \leq V_{in,CM} \leq V_{DD} - R_D \frac{I_{SS}}{2} + V_{TH3}$$

• DM small signal gain: $-G_m * R_{out}$

增益等于输入管 g_m * 输出节点的阻抗 (上下并联)


• CM small signal gain: $(g_m / (1 + g_m r_{ss})) * R_{out}$

• OTA with five transistors

 

$$A_v = -g_{mN} (g_{mP}^{-1} \parallel r_{on} \parallel r_{op}) = -\frac{g_{mN}}{g_{mP}} = \sqrt{\frac{\mu_n (\frac{W}{L})_n}{\mu_p (\frac{W}{L})_p}}$$
 
$$\sqrt{2 \mu_n C_{ox} (\frac{W}{L})_n I} = g_m$$



双端输入双端输出: $A_v = g_m R_D$

单端输入双端输出: $A_v = g_m R_D$


双端输入单端输出: $A_v = \frac{1}{2} g_m R_D$

主要内容 (9) 运算放大器一般性了解即可

- Ideal Opamp
- DC gain and dominant pole of single stage, telescopic and folded-cascade amplifier
- DC gain and two poles of two stage amplifier, after miller compensation
- Input and output range
(every transistor in saturation)
- Speed and Slew rate
(small signal and large signal behavior)

主要内容 (10) Elmore delay

 - Wire parasitics
 - Capacitance, Resistance, Inductance
- Wire models (lumped, distributed)




$$\tau(V_{out}) = \frac{rcL^2}{2}$$

$$\tau_D = R_s C_w + \frac{R_w C_w}{2} = R_s C_w + 0.5 r_w c_w L^2$$

$$t_p = 0.69 R_s C_w + 0.38 R_w C_w$$


传输线定理

 

$$\tau_{Di} = C_1 r_1 + C_2 (r_1 + r_2) + \dots + C_i (r_1 + r_2 + \dots + r_i)$$

$$\tau_{Di} = C_1 r_{eq} + 2C_2 r_{eq} + 3C_3 r_{eq} + \dots + iC_i r_{eq}$$

主要内容 (10) Elmore delay of gates

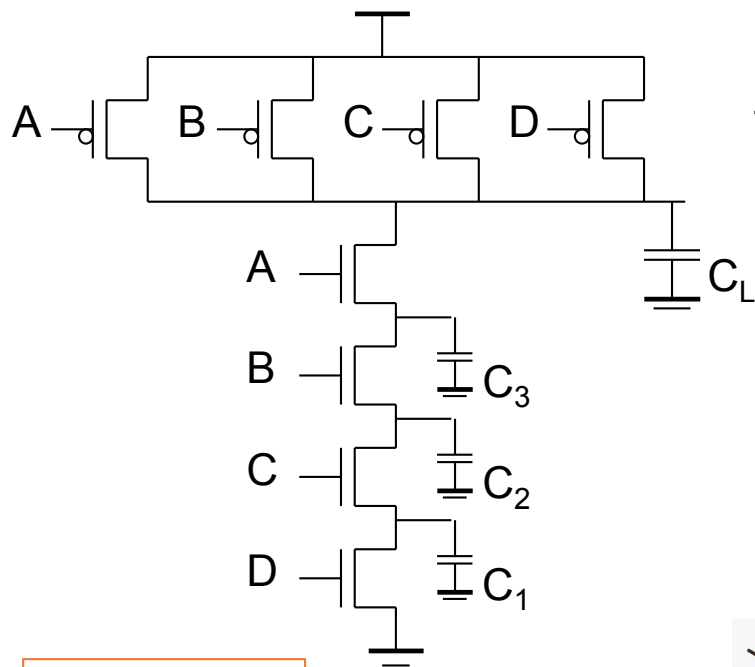

Distributed RC model (Elmore delay)

$$t_{pHL} = 0.69 [R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3 + (R_1 + R_2 + R_3 + R_4) C_L]$$


NMOS: same size R_{eqn}

$$t_{pHL} = 0.69 R_{eqn} (C_1 + 2C_2 + 3C_3 + 4C_L)$$

the worst-case



 - ❑ The number of transistor required to implement an N fan-in is $2N$ => area, capacitance
- ❑ Propagation delay deteriorates rapidly as a function of fan-in (# of inputs) – **Quadratically**



主要内容 (11)

$$2f = f_{sw}$$


- Digital power consumption: $P_{\text{switching}} = \alpha C V_{DD}^2 f$

- Inverter: 反相器的阈值电压和 $(W/L)_{\text{pmos}} / (W/L)_{\text{nmos}}$ 成正比

- Delay: 反相器延时 $t_p = t_{p0} (1 + C_{\text{ext}} / \gamma C_g)$

$$V_M = \frac{r \cdot V_{DD}}{1+r}$$

$$V_M = V_{in} = V_{out}$$


 


$$N = \ln(F)$$

$$f = 2.71828 = e$$

主要内容 (12)

 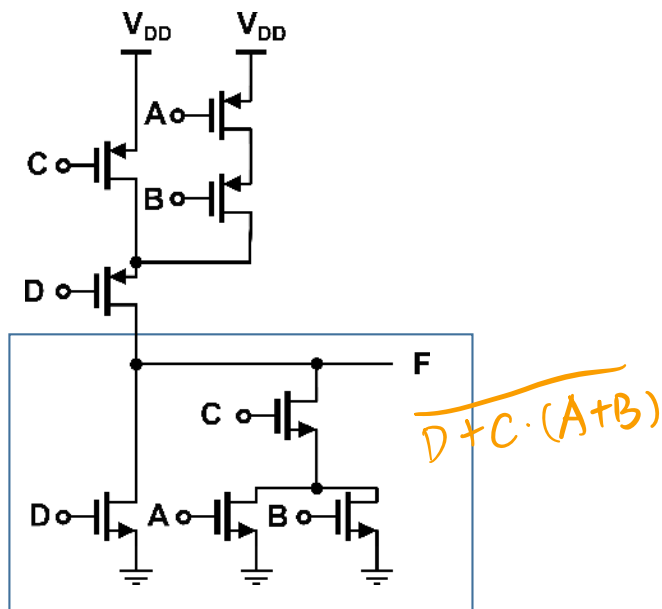
- 传输门, 组合逻辑, 动态逻辑 (两者的定义与区别)
- 从逻辑表达式 到电路拓扑图 到版图




Analog Example (1)

A single-stage amplifier is shown in Fig.4, assuming $\gamma=0$, $\lambda \neq 0$ and $r_o \gg 1/g_m$.

 - (1) Please give its **equivalent small-signal circuits**. And calculate the symbolic small-signal **output resistance**, r_{out} , and the **voltage gain**, A_v ;
- (2) If the width W_1 of M_1 is increased, how does the gain change? Explain the reason;



 (1) $r_{out} = r_o // R_o$ (2 分) , $A_v = g_m \times R_{out} = g_m \times (r_o // R_o)$ (2 分)



(4 分, 按实际绘图情况给分), 没有画 r_o 扣 1 分

(2) $g_m = K \frac{W_1}{L_1} (V_{GS} - V_{TH})(1 + \lambda V_{DS})$, $r_o = \frac{1}{\lambda I_D} = \frac{2}{\lambda K \frac{W_1}{L_1} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})}$

$$A_v = g_m \frac{r_o R_o}{r_o + R_o} = K \left(\frac{W_1}{L_1} \right) (V_{GS} - V_{TH})(1 + \lambda V_{DS}) \frac{R_o}{1 + \lambda I_D R_o}$$

$$= K(V_{GS} - V_{TH})(1 + \lambda V_{DS}) R_o \left(\frac{1}{\frac{L_1}{W_1} + \frac{1}{2} \lambda K R_o (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})} \right)$$

所以总体的增益是增加的 (2 分)


Analog Example (2)

In the circuit of Fig 6.3, assume that $I_{SS}=1\text{mA}$, $V_{DD}=3\text{V}$ and $W/L=50/0.5$ for all the transistors. And $I_{D5}=I_{D6}=0.8 (I_{SS}/2)$. Assuming $\lambda \neq 0$.

- Determine the **symbolic** voltage gain.
- Calculate V_b .
- What is the input common mode voltage range

$$a) \quad A_V \approx -\frac{g_{m1}}{g_{m3}} = -\sqrt{\frac{K_n I_{D1}}{K_p I_{D3}}} = -\sqrt{\frac{134 \times 0.5 I_{SS}}{50 \times 0.2 \frac{I_{SS}}{2}}} = -3.66$$

$$b) \quad I_{D5} = I_{D6} = 0.8 \frac{I_{SS}}{2} = 0.4\text{mA}, V_b = V_{DD} - V_{SG5} = V_{DD} - |V_{TH}| - \sqrt{\frac{2I_{D5}}{K_p \frac{W}{L}}} = 1.8\text{V}$$

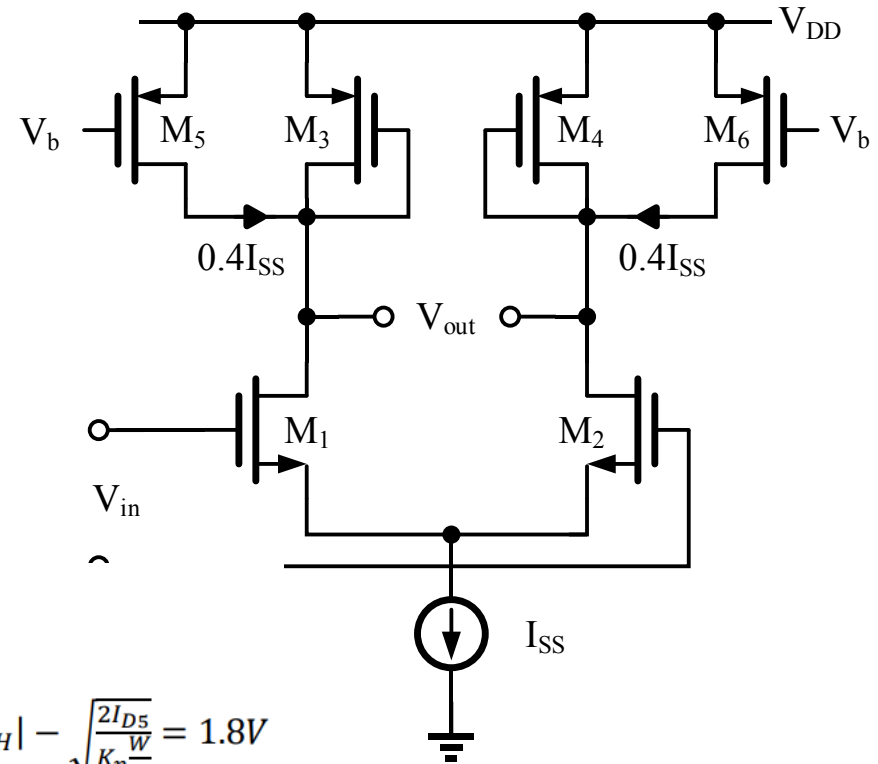



Digital Example

(1) Please describe the concept of “**static logic circuit**” and “**dynamic logic circuit**” in digital circuits;

 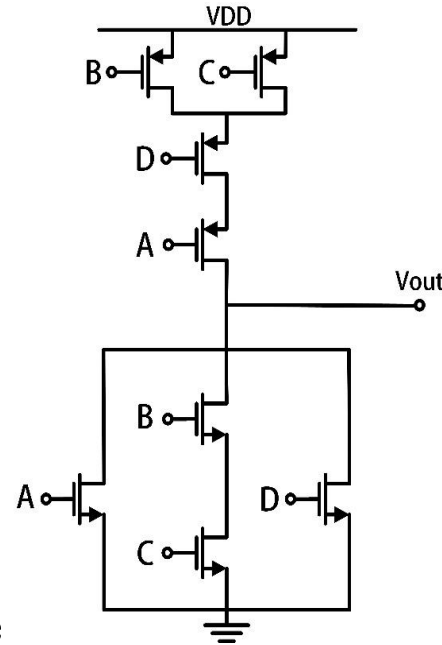(2) Sketch 4-input gates $F = \overline{A + BC + D}$ using the circuit techniques of **static CMOS** and **dynamic gates**, respectively.

The *static* circuits class, which each gate output is connected to either VDD or Vss via a low-resistance path at every point in time.

The *dynamic* circuit class, which relies on temporary storage of signal values on the capacitance of high-impedance circuit nodes.



祝大家考试顺利 假期愉快

